
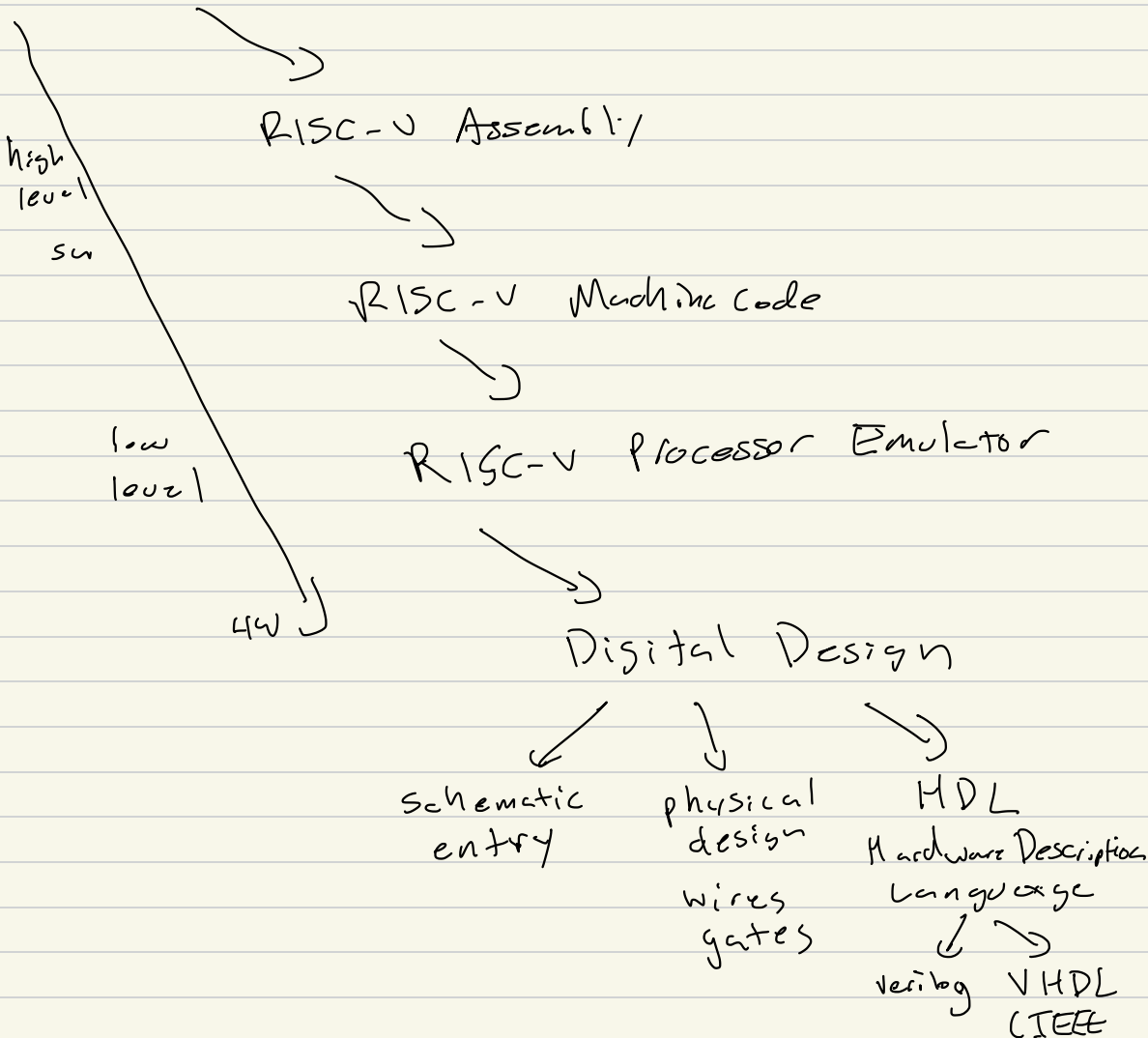


Combinational Logic / Sequential Logic


C code / Rust code

 

SW



Analog \rightarrow Digital

 

power source



wires

devices \rightarrow gates

AND

OR

NOT

  

C / Rust

$$r = a \& b$$

$$r = a | b$$

$$r = \sim b$$

Bo-lean

Algebra

$$r = a \cdot b$$

$$r = a + b$$

$$r = \bar{a}$$

Logic

$$r = a \wedge b$$


$$r = a \vee b$$

$$r = \neg a$$

a	b	r
0	0	0
0	1	0
1	0	0
1	1	1


a	b	r
0	0	0
0	1	1
1	0	1
1	1	1

a	r
0	1
1	0

 

$$r = (a \cdot b) + (c \cdot d)$$

Goal: 8-bit adder

 



Sum-of-products

sum of tw. 1-bit values

$$\text{sum} = a \oplus b$$

a	b	sum
0	0	0
0	1	1
1	0	1
1	1	0
  
$$\text{sum} = (\bar{a} \cdot b) + (a \cdot \bar{b})$$




sum-of-products

- 1) define your function (on binary inputs)
- 2) Build the truth table
- 3) Identify rows with output = 1
- 4) Construct product terms for each row
 - a) don't invert if input is 1
 - b) invert if input is 0
- 5) sum (+) all product terms


1 bit full adder

a	b	c _{in}	sum	cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 

$$\text{sum} = (\bar{a} \cdot \bar{b} \cdot c_{in}) + (\bar{a} \cdot b \cdot \bar{c}_{in}) + (a \cdot \bar{b} \cdot \bar{c}_{in}) + (a \cdot b \cdot c_{in})$$

$$\text{cout} = \dots$$

 


4 bit adder - 4 bit Ripple Carry Adder


a $a_3 a_2 a_1 a_0$

b $b_3 b_2 b_1 b_0$
 
$$\begin{array}{r}
 0101 \\
 + 0011 \\
 \hline
 1000
 \end{array}$$



4 bit ripple carry adder

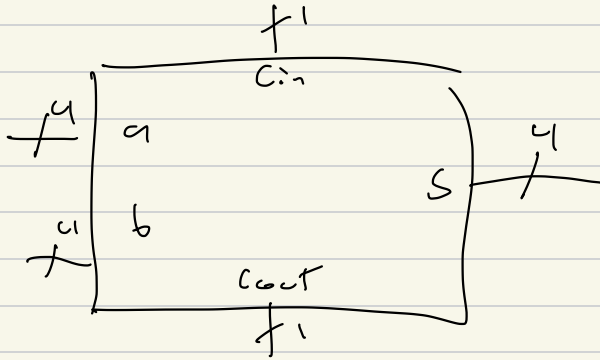

Goal: N-bit register

state

SR Latch

